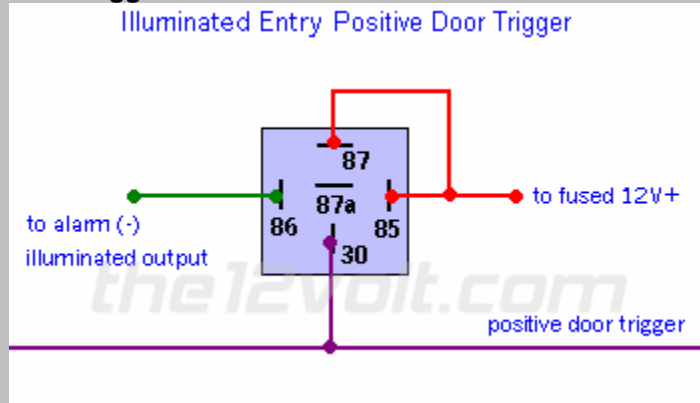


Illuminated Entry for Vehicles with Positive Door Triggers

When you unlock or disarm your vehicle with an alarm or keyless and have an output (usually 30 - 60 seconds long), and have positive door triggers, the output is connected to a relay as shown. For negative door triggers see [next](#).



Illuminated Entry for Vehicles with Negative Door Triggers

When you unlock or disarm your vehicle with an alarm or keyless and have an output (usually 30 - 60 seconds long), and have negative door triggers, the output is connected to a relay as shown. For positive door triggers see [above](#).

