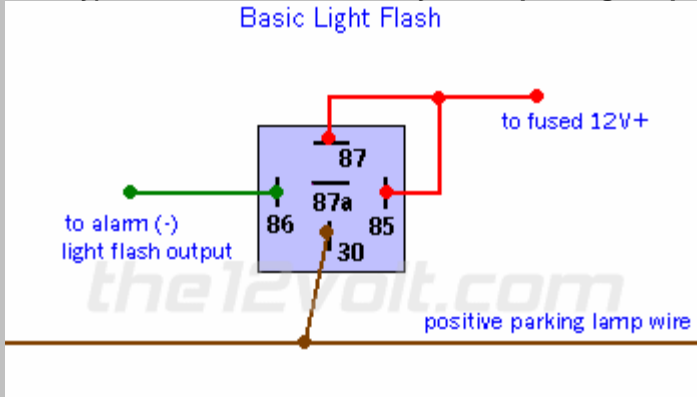


Basic Light Flash


If the alarm or keyless entry you are installing has a light flash output other than one (with an on board relay) that is connected directly to the parking lamps. The connections are shown




below.

Two Wire Light Flash

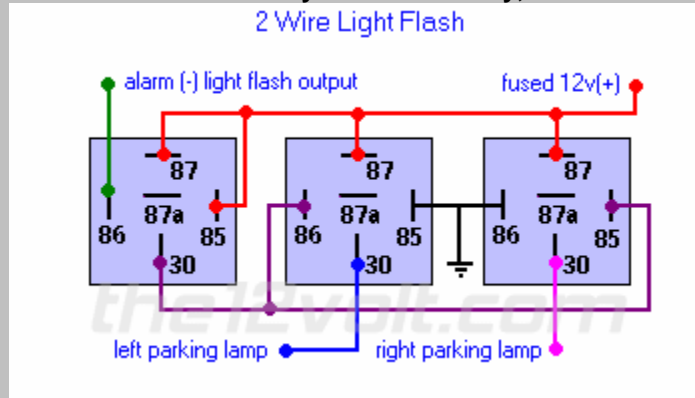
Most commonly found on German automobiles, separate left and right parking lamp circuits will require at least one more SPDT relay. If your alarm or keyless entry's negative output can not energize the coils of more than one relay simultaneously, the connections are as shown.



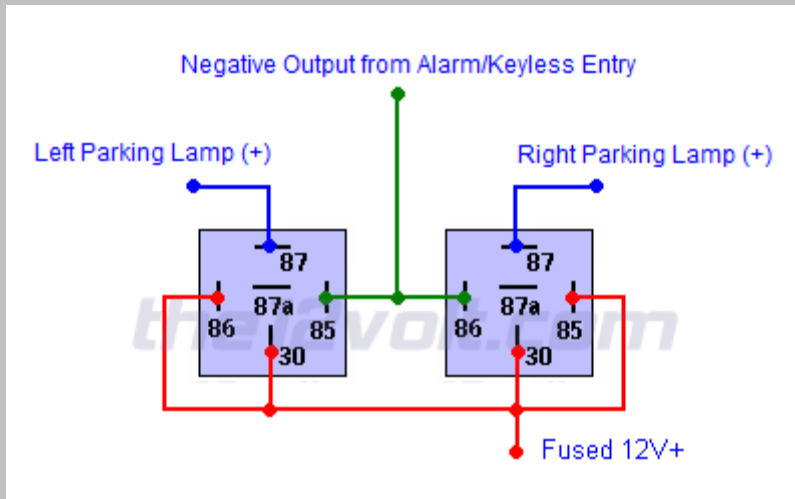If your alarm or keyless entry's negative output can energize the coils of two relays, use the following diagram.




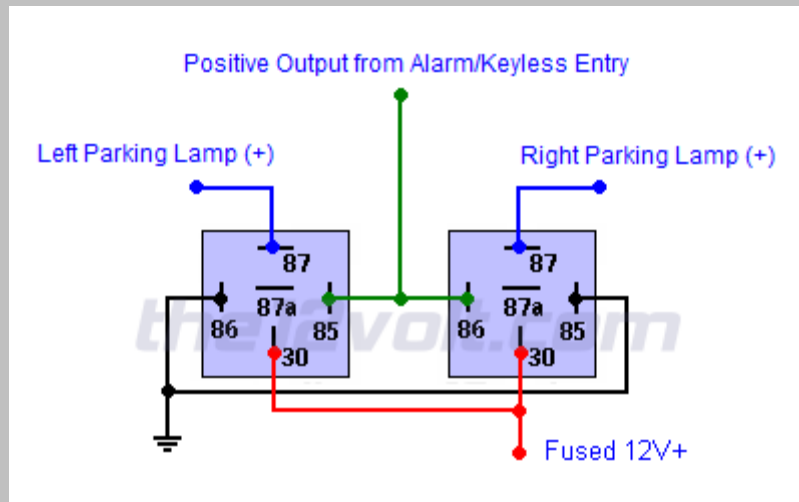If your alarm or keyless entry has an on board relay with a positive output, use the following diagram.



Adding Light Flash with Siren Output

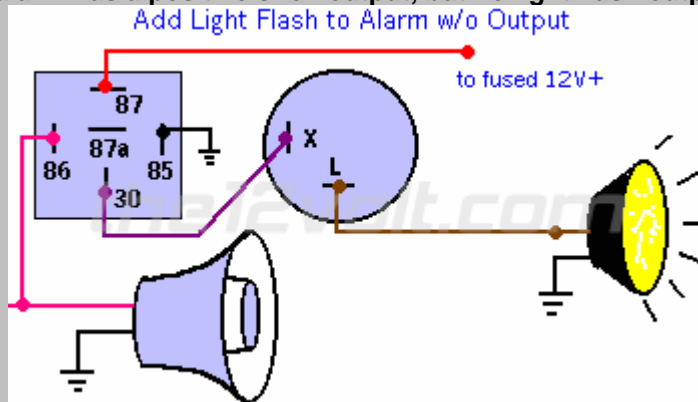If your alarm has a positive siren output, but no light flash output, the connections are as



shown.